

Boolean Algebra

BOOLEAN ALGEBRA

- **Formal logic:** In formal logic, a statement (proposition) is a declarative sentence that is either true(1) or false (0).
- It is easier to communicate with computers using formal logic.
- **Boolean variable:** Takes only two values – either true (1) or false (0).
- They are used as basic units of formal logic.

Boolean function and logic diagram

- **Boolean function:** Mapping from Boolean variables to a Boolean value.
- **Truth table:**
 - Represents relationship between a Boolean function and its binary variables.
 - It enumerates all possible combinations of arguments and the corresponding function values.

Boolean function and logic diagram

- **Boolean algebra:** Deals with binary variables and logic operations operating on those variables.
- **Logic diagram:** Composed of graphic symbols for logic gates.
 - A simple circuit sketch that represents inputs and outputs of Boolean functions.

Boolean Algebra

- **Boolean Algebra:** a useful mathematical system for specifying and transforming logic functions.
- We study Boolean algebra as a foundation for designing and analyzing digital systems!

Logical Operations

- The three basic logical operations are:
 - AND
 - OR
 - NOT
- AND is denoted by a dot (\cdot).
- OR is denoted by a plus ($+$).
- NOT is denoted by an overbar ($\bar{\quad}$), a single quote mark ($'$) after, or (\sim) before the variable.

Operator Definitions

Operations are defined on the values "0" and "1" for each operator:

AND	OR	NOT
$0 \cdot 0 = 0$	$0 + 0 = 0$	$\bar{0} = 1$
$0 \cdot 1 = 0$	$0 + 1 = 1$	$\bar{1} = 0$
$1 \cdot 0 = 0$	$1 + 0 = 1$	
$1 \cdot 1 = 1$	$1 + 1 = 1$	

BASIC IDENTITIES OF BOOLEAN ALGEBRA

- A Boolean algebra is a closed algebraic system containing a set K of two or more elements and the two operators \cdot and $+$ which refer to logical AND and logical OR

Basic Identities of Boolean Algebra (Existence of 1 and 0 element)

- (1) $x + 0 = x$
- (2) $x \cdot 0 = 0$
- (3) $x + 1 = 1$
- (4) $x \cdot 1 = x$

Basic Identities of Boolean Algebra (Existence of complement)

- (5) $x + x' = 1$
- (6) $x \cdot x' = 0$
- (7) $x + x'' = x$
- (8) $x \cdot x'' = x$

Basic Identities of Boolean Algebra (Commutativity):

- (9) $x + y = y + x$
- (10) $xy = yx$

Basic Identities of Boolean Algebra (Associativity):

- (11) $x + (y + z) = (x + y) + z$
- (12) $x(yz) = (xy)z$

Basic Identities of Boolean Algebra (Distributivity):

$$(13) x (y + z) = xy + xz$$

$$(14) x + yz = (x + y)(x + z)$$

Basic Identities of Boolean Algebra (DeMorgan's Theorem)

$$(15) (x + y)' = x' y'$$

$$(16) (xy)' = x' + y'$$

Basic Identities of Boolean Algebra (Involution)

$$(17) (x')' = x$$

Some Properties of Boolean Algebra

- Boolean Algebra is defined in general by a set B that can have more than two values
- A two-valued Boolean algebra is also known as Switching Algebra. The Boolean set B is restricted to 0 and 1. Switching circuits can be represented by this algebra.

Some Properties of Boolean Algebra

- The dual of an algebraic expression is obtained by interchanging $+$ and \cdot and interchanging 0's and 1's.
- The identities appear in dual pairs. When there is only one identity on a line the identity is self-dual, i. e., the dual expression = the original expression.
- Sometimes, the dot symbol \cdot (AND operator) is not written when the meaning is clear

Dual of a Boolean Expression

Example: $F = (A + \bar{C}) \cdot B + 0$

$$\text{dual } F = (\bar{A} \cdot \bar{C} + B) \cdot 1 = \bar{A} \cdot \bar{C} + B$$

Example: $G = X \cdot Y + (\bar{W} + \bar{Z})$

$$\text{dual } G = (X+Y) \cdot (\bar{W} \cdot \bar{Z}) = (X+Y) \cdot \overline{(\bar{W} + \bar{Z})}$$

Example: $H = A \cdot B + A \cdot C + B \cdot C$

$$\text{dual } H = (A+B) \cdot (A+C) \cdot (B+C)$$

Boolean Operator Precedence

- The order of evaluation is:
 1. Parentheses
 2. NOT
 3. AND
 4. OR
- Consequence: Parentheses appear around OR expressions
- Example: $F = A(B + C)(C + D)$ —

Function Minimization using Boolean Algebra

Examples:

- (a) $a + ab = a(1+b)=a$
- (b) $a(a + b) = a.a + ab = a + ab = a(1+b)=a$.
- (c) $a + ab = (a + a)(a + b) = 1(a + b) = a + b$
- (d) $a(a + b) = a.a + ab = 0 + ab = ab$

Try

- $F = abc + abc' + a'c$

The other type of question

Show that;

$$1- ab + ab' = a$$

$$2- (a + b)(a + b') = a$$

$$1- ab + ab' = a(b+b') = a.1 = a$$

$$\begin{aligned}
 2- (a + b)(a + b') &= a.a + a.b' + a.b + b.b' \\
 &= a + a.b' + a.b + 0 \\
 &= a + a.(b' + b) + 0 \\
 &= a + a.1 + 0 \\
 &= a + a = a
 \end{aligned}$$

More Examples

- Show that;
 - (a) $ab + ab'c = ab + ac$
 - (b) $(a + b)(a + b' + c) = a + bc$
- (a) $ab + ab'c = a(b + b'c) = a((b+b').(b+c)) = a(b+c) = ab+ac$
- (b) $(a + b)(a + b' + c) = (a.a + a.b' + a.c + ab + b.b' + bc) = \dots$

DeMorgan's Theorem

$$(a + b)' = a'b$$

$$(ab)' = a' + b'$$

Generalized DeMorgan's Theorem

$$(a + b + \dots + z)' = a'b' \dots z'$$

$$(a \cdot b \dots z)' = a' + b' + \dots + z'$$

DeMorgan's Theorem

$$F = ab + c'd'$$

$$F' = ??$$

$$F = ab + c'd' + b'd$$

$$F' = ??$$

DeMorgan's Theorem

Show that: $(a + b \cdot c)' = a' \cdot b' + a' \cdot c'$

More DeMorgan's example

Show that: $(a(b + z(x + a')))' = a' + b' (z' + x')$

$$\begin{aligned} (a(b + z(x + a')))' &= a' + (b + z(x + a'))' \\ &= a' + b' (z(x + a'))' \\ &= a' + b' (z' + (x + a'))' \\ &= a' + b' (z' + x'(a'))' \\ &= a' + b' (z' + x'a) \\ &= a' + b' z' + b'x'a \\ &= (a' + b'x'a) + b' z' \\ &= (a' + b'x')(a + a') + b' z' \\ &= a' + b'x' + b' z' \\ &= a' + b' (z' + x') \end{aligned}$$

Truth Table

- Logic diagram:** a graphical representation of a circuit
 - Each type of gate is represented by a specific graphical symbol
- Truth table:** defines the function of a gate by listing all possible input combinations that the gate could encounter, and the corresponding output

Truth Tables

- Example: Truth tables for the basic logic operations:

AND		
X	Y	Z = X·Y
0	0	0
0	1	0
1	0	0
1	1	1

OR		
X	Y	Z = X+Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT	
X	Z = \overline{X}
0	1
1	0

Truth Tables – Cont'd

- Used to evaluate any logic function
- Consider $F(X, Y, Z) = XY + \bar{Y}Z$

X	Y	Z	XY	\bar{Y}	$\bar{Y}Z$	$F = XY + \bar{Y}Z$
0	0	0	0	1	0	0
0	0	1	0	1	1	1
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	1	0	0
1	0	1	0	1	1	1
1	1	0	1	0	0	1
1	1	1	1	0	0	1

Logic Gates

Logic Gates

- A logic gate is an elementary building block of a digital circuit .
- Most logic gates have two inputs and one output.
- At any given moment, every terminal is in one of the two binary conditions *low* (0) or *high* (1), represented by different voltage levels.

Boolean Constants and Variables

- Boolean 0 and 1 do not represent actual numbers but instead represent the state, or logic level.

Logic 0	Logic 1
False	True
Off	On
Low	High
No	Yes
Open switch	Closed switch

Three Basic Logic Operations

- OR
- AND
- NOT
- Other derived logic operations
 - NOR
 - NAND
 - XOR
 - XNOR

Truth Tables

- A truth table is a means for describing how a logic circuit's output depends on the logic levels present at the circuit's inputs

Inputs		Output
A	B	x
0	0	1
0	1	0
1	0	1
1	1	0

OR Gate

- The *OR gate* gets its name from the fact that it behaves after the fashion of the logical inclusive "or."
- The output is "true" if either or both of the inputs are "true."
- If both inputs are "false," then the output is "false."

OR Operation

- Boolean expression for the OR operation:
 $x = A + B$
- The above expression is read as "x equals A OR B"

A	B	x = A + B
0	0	0
0	1	1
1	0	1
1	1	1

(a) (b)

OR Gate

- An OR gate is a gate that has two or more inputs and whose output is equal to the OR combination of the inputs.

A	B	C	x = A + B + C
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

The switch equivalent of an OR gate

AND Gate

- The *AND gate* is so named because, if 0 is called "false" and 1 is called "true,"
- the gate acts in the same way as the logical "and" operator.

AND Operation

- Boolean expression for the AND operation:
 $x = A \cdot B$
- The above expression is read as "x equals A AND B"

A	B	x = A · B
0	0	0
0	1	0
1	0	0
1	1	1

(a) (b)

AND Gate

- An AND gate is a gate that has two or more inputs and whose output is equal to the AND product of the inputs

A	B	C	x = ABC
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

The switch equivalent of an AND gate

NOT Operation

- A logical *inverter*, sometimes called a *NOT gate* to differentiate it from other types of electronic inverter devices,
- has only one input.
- It reverses the logic state.

NOT Operation

Boolean expression for the NOT operation:
 $x = \bar{A}$

- The above expression is read as "x equals the inverse of A"
- Also known as inversion or complementation.
- Can also be expressed as: A'

A	x = \bar{A}
0	1
1	0

Presence of small circle always denotes inversion

The switch equivalent of a NOT gate

NOR gate

- The *NOR gate* is a combination OR gate followed by an inverter.
- Its output is "true" if both inputs are "false."
- Otherwise, the output is "false."

NOR Gate

Boolean expression for the NOR operation:

X

OR		NOR	
A	B	A + B	$\overline{A + B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

The NAND gate

- The *NAND gate* operates as an AND gate followed by a NOT gate.
- It acts in the manner of the logical operation "and" followed by negation.
- The output is "false" if both inputs are "true."
- Otherwise, the output is "true."

NAND Gate

Boolean expression for the NAND operation:

X

AND		NAND	
A	B	AB	\overline{AB}
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

alternative symbol for NOR function


XOR (exclusive-OR) gate

- The *XOR (exclusive-OR) gate* acts in the same way as the logical "either/or."
- The output is "true" if either, but not both, of the inputs are "true."
- The output is "false" if both inputs are "false" or if both inputs are "true."

XOR (exclusive-OR) gate

- Another way of looking at this circuit is to observe that the output is 1 if the inputs are different, but 0 if the inputs are the same.

XOR (exclusive-OR) gate

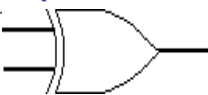


Input 1	Input 2	Output
0	0	0
0	1	1
1	0	1
1	1	0

XNOR (exclusive-NOR) gate

- The XNOR (exclusive-NOR) gate is a combination XOR gate followed by an inverter.
- Its output is "true" if the inputs are the same, and "false" if the inputs are different

XNOR (exclusive-NOR) gate





Input 1	Input 2	Output
0	0	1
0	1	0
1	0	0
1	1	1

Describing Logic Circuits Algebraically


- Any logic circuits can be built from the three basic building blocks: OR, AND, NOT
- Example 1: $x = A \cdot B + C$
- Example 2: $x = \overline{(A+B)C}$
- Example 3: $\overline{x} = (\overline{A+B})$
- Example 4: $x = \overline{ABC} (A+D)$


Examples 1,2

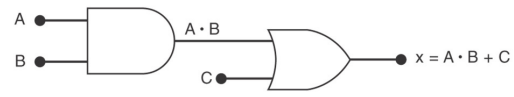
(a) 

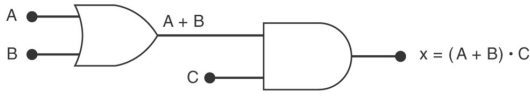(b) 

Examples 3

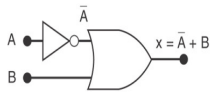
(a) 

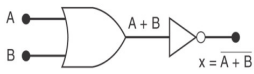(b) 

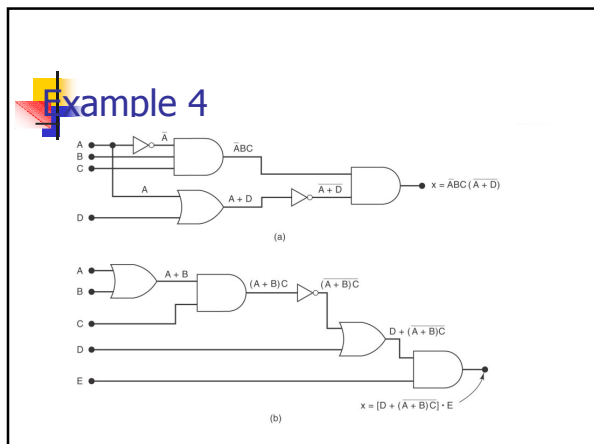



- ### Evaluating Logic Circuit Output
- Evaluation rule for Boolean expression
 - 1) Perform all inversions of single terms
 - 2) Perform all operations within parentheses
 - 3) Perform an AND operation before an OR operation
 - 4) If an expression has a bar over it, perform the expression first and then invert the result

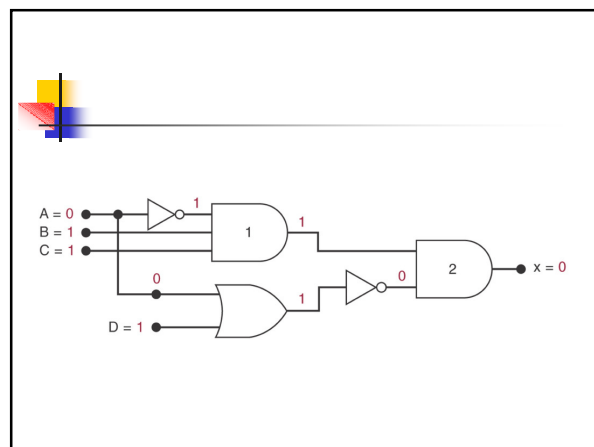- ### Evaluating Logic-Circuit Outputs
- $x = ABC(A+D)$
 - Determine the output x given A=0, B=1, C=1, D=1.
 - Can also determine output level from a diagram



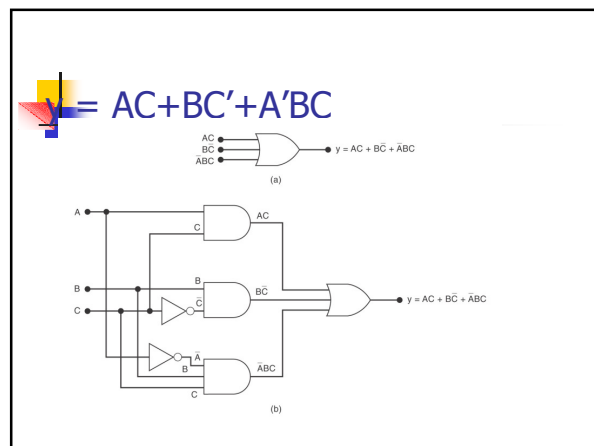- ### Implementing Circuits from Boolean Expressions
- $y = AC+BC'+A'BC$
 - $x=(A+B)(B'+C)$



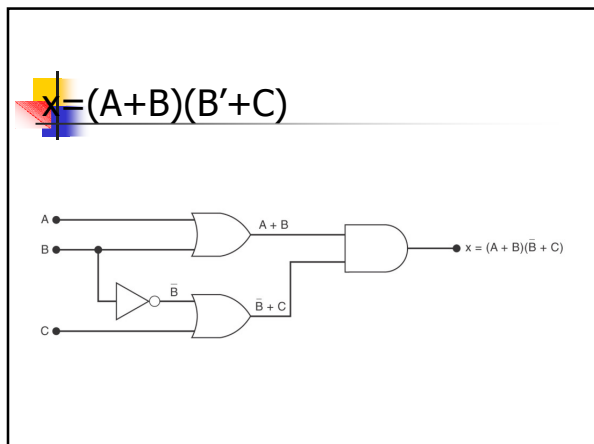

Alternate Logic Symbols

- Sometimes the logic of a circuit is more easily understood if an alternative gate shape is used.
- DeMorgan=s Theorem** can be used to determine equivalent logic gates.

Alternate Logic Symbols

- Rules:**
 - Change the gate shape (AND ==> OR; OR ==> AND).
 - Change the bubbles (add where missing; remove if present).

